
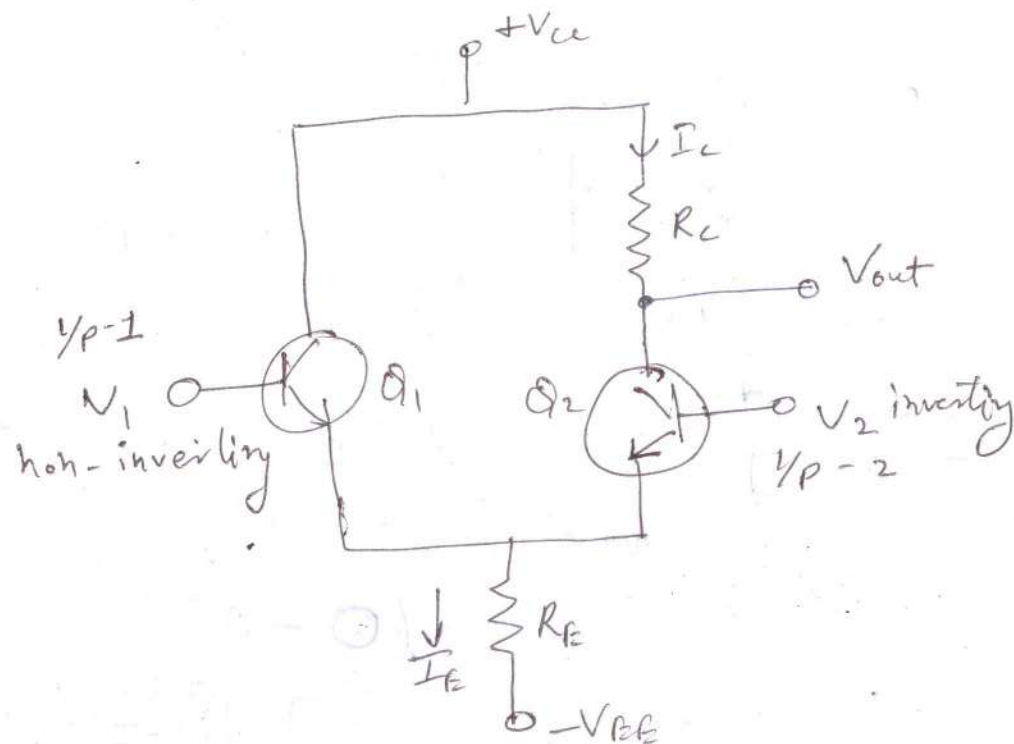


Basic Operational Amplifier (1)

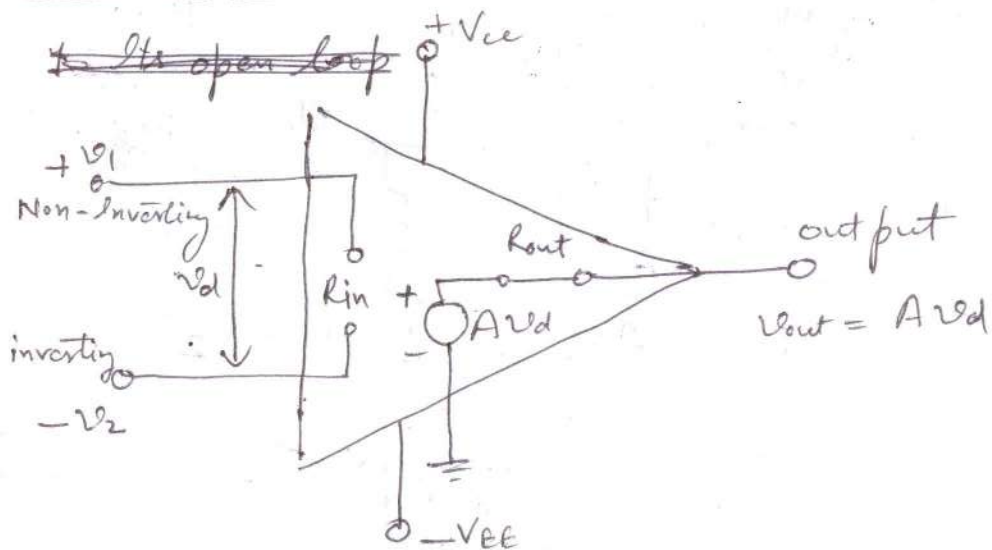


IDEAL OP-AMP




1. Its open loop gain A is infinite.
2. Its i/p resistance R_{in} is ~~zero~~ infinite.
3. Its out impedance R_{out} is zero.
4. Infinite frequency bandwidth.
5. Drift of characteristics with temperature is nil.
6. Common mode rejection ratio (CMRR) is infinite.
7. Slew rate is infinite.
8. Offset voltage is zero.

Voltage Transfer Curve

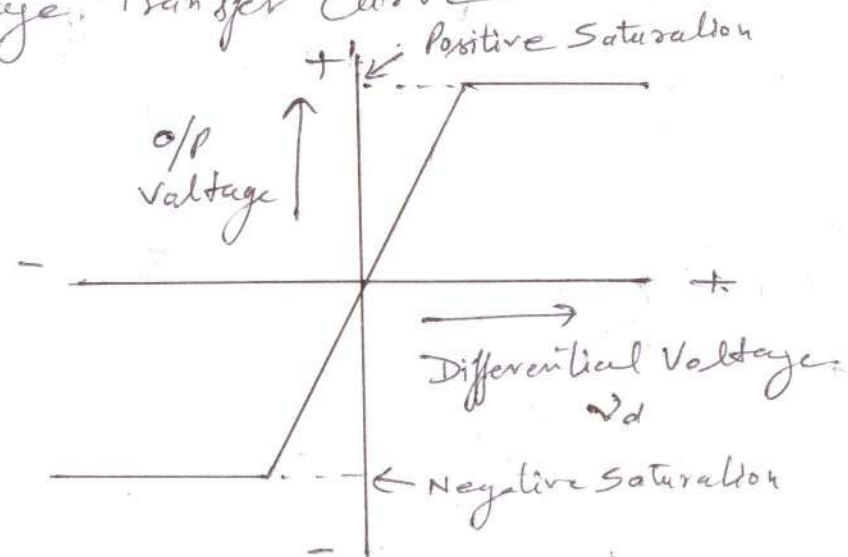


Practical OP-AMP

(3)

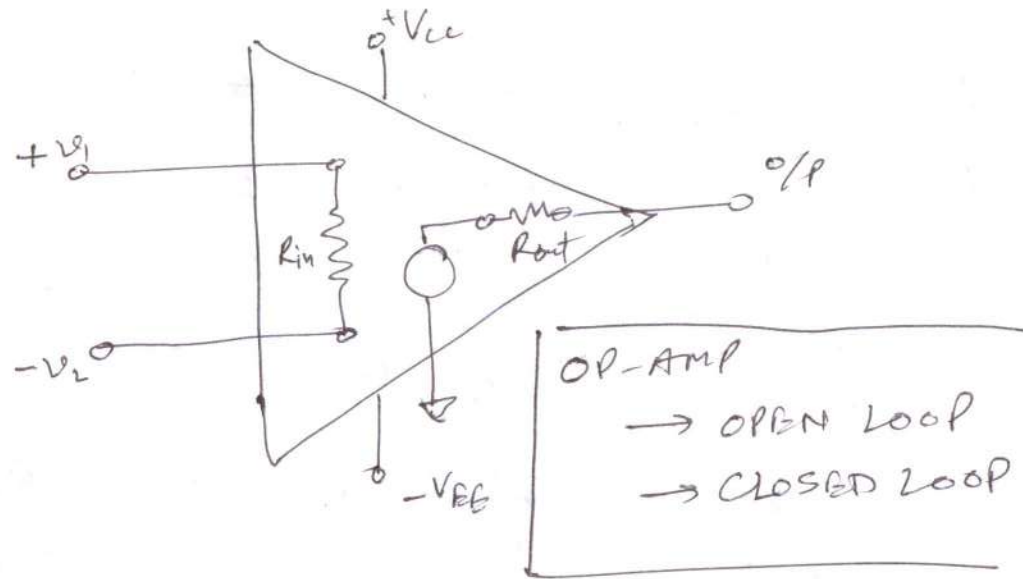

2 Inverting Amp

(4)

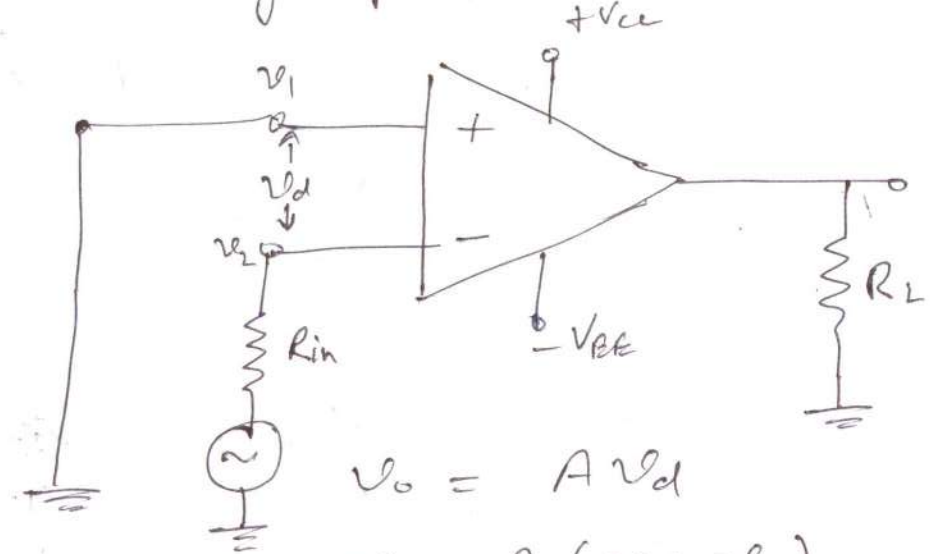

$$v_o = A v_d$$

$$v_o = A (v_1 - v_2)$$


$$= A (0 - v_2)$$

$$v_o = -A v_2$$


$$v_o = -A v_{in}$$

Open Loop OP-AMP Configurations:

1. Differential Amp.

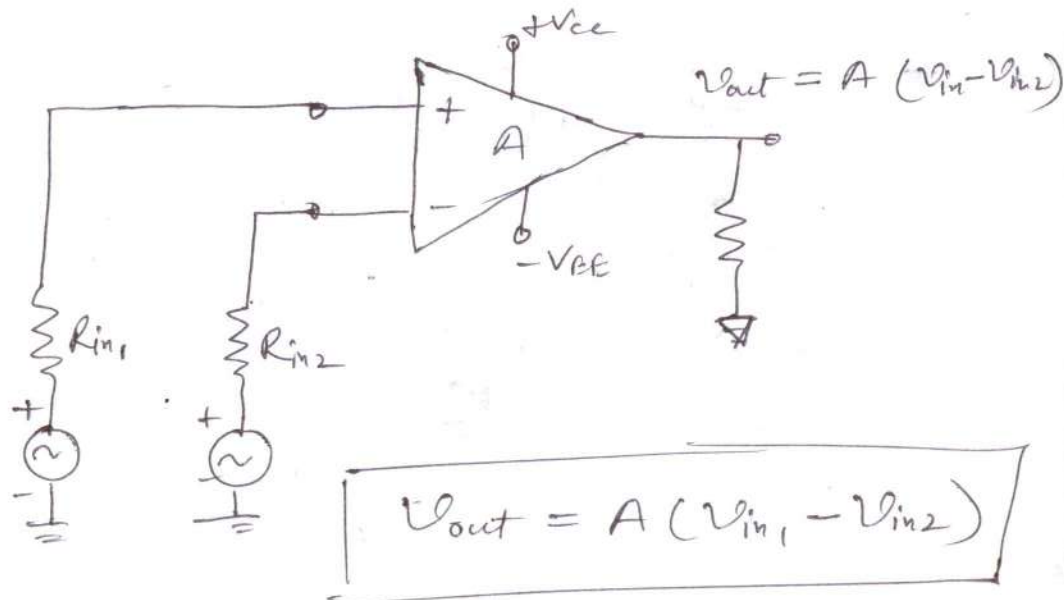

3. Non Inverting Amp

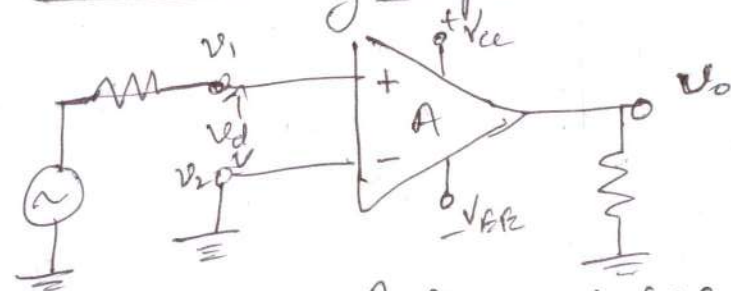

$$v_o = A v_d = A (v_1 - v_2)$$


$$v_o = A (v_1 - 0)$$

$$v_o = A v_{in}$$

$$v_o = A v_{in}$$

Closed loop op-amp configurations

1. Inverting Amp.

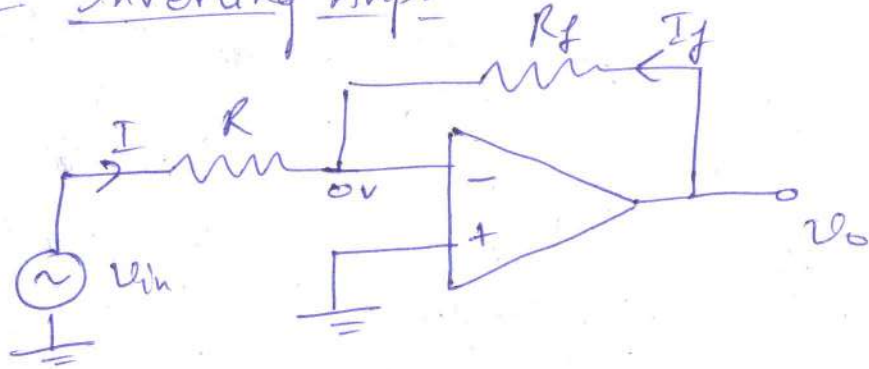

From the figure.

$$I + I_f = 0$$

$$\frac{v_{in} - 0}{R} + \frac{v_o - 0}{R_f} = 0$$

$$\frac{v_{in}}{R} + \frac{v_o}{R_f} = 0$$


$$\frac{v_o}{R_f} = -\frac{v_{in}}{R}$$

$$v_o = -\frac{R_f}{R} v_{in}$$

$$\boxed{v_o = -A_f v_{in}}$$

where $A_f = \frac{R_f}{R}$

2. Non-Inverting Amp.

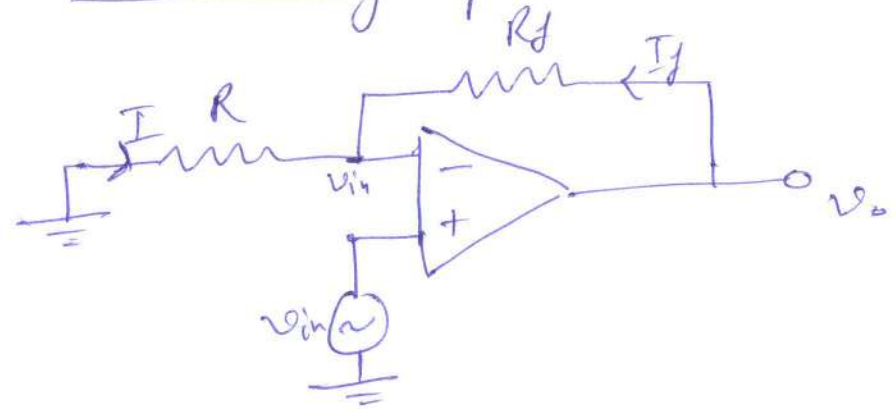

$$I + I_f = 0$$

$$\frac{0 - v_{in}}{R} + \frac{v_o - v_{in}}{R_f} = 0$$

$$-\frac{v_{in}}{R} + \frac{v_o}{R_f} - \frac{v_{in}}{R_f} = 0$$

$$\frac{v_o}{R_f} = \frac{v_{in}}{R_f} + \frac{v_{in}}{R}$$

$$v_o = v_{in} \left(\frac{R_f}{R_f} + \frac{R_f}{R} \right)$$

$$v_o = v_{in} \left(1 + \frac{R_f}{R} \right)$$

$$\boxed{v_o = A_f v_{in}}$$

where $A_f = \left(1 + \frac{R_f}{R} \right)$

- ① Design a non-inverting amplifier ckt that is capable of providing a voltage gain of 10. Assume an ideal op-amp. (~~ideal op-amp~~; resistance should not exceed $30\text{ k}\Omega$)

Solⁿ for non-inverting op-amp

$$A_f = 1 + \frac{R_f}{R}$$

$$10 = 1 + \frac{R_f}{R}$$

$$\frac{R_f}{R} = 10 - 1 = 9$$

$$R_f = 9R \quad \text{--- ①}$$

if we take R is as $3\text{ k}\Omega$

$$R_f = 9 \times 3 = 27\text{ k}\Omega$$

$$\boxed{R_f = 27\text{ k}\Omega}$$

which is less than $30\text{ k}\Omega$, ANS

- ② In the given figure, the variable resistance varies from 0 to $100\text{ k}\Omega$. Find out the maximum and the minimum closed loop voltage gain.

Solⁿ

$$R = 2\text{ k}\Omega$$

$$R_f(\text{min}) = 0\text{ k}\Omega$$


$$R_f(\text{max}) = 100\text{ k}\Omega$$

closed loop voltage gain

$$A_f = 1 + \frac{R_f}{R}$$

$$A_{f(\text{max})} = 1 + \frac{100}{2} = 1 + 50 = 51 \text{ ANS}$$
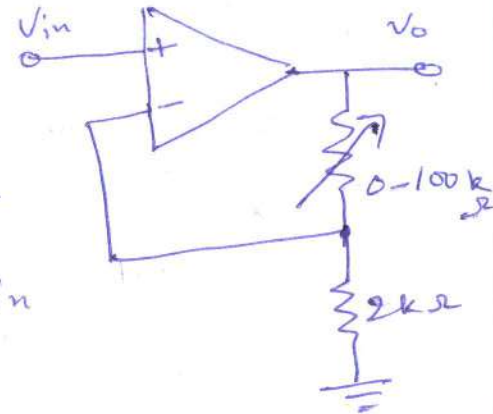
$$A_{f(\text{min})} = 1 + \frac{0}{2} = 1 \text{ ANS}$$



(3)

③ An Inverting amplifier has $R_f = 500 \text{ k}\Omega$ and $R_i = 5 \text{ k}\Omega$. Determine the amplifier ckt voltage gain, input resistance and output resistance. Also Determine the output voltage and input current if the input voltage is ~~0.1~~ 0.1 V .
(Assume op-amp to be ideal one.)

Sol $R = 5 \text{ k}\Omega$; $R_f = 500 \text{ k}\Omega$

$$V_{in} = 0.1 \text{ V}$$

$$\text{Voltage gain } A_f = -\frac{R_f}{R} = -\frac{500 \text{ k}\Omega}{5 \text{ k}\Omega} = -100 \text{ ANS}$$

$$\text{i/p resistance } R_{in} = R = 5 \text{ k}\Omega \text{ ANS}$$

$$\text{o/p resistance } R_{out} = 0 \text{ ANS}$$


$$\text{output voltage } V_o = A_f V_{in} = -100 \times 0.1$$

$$\boxed{V_o = -10 \text{ V}} \text{ ANS}$$

$$\text{input current } I_{in} = \frac{V_{in}}{R} = \frac{0.1}{5 \times 1000} =$$

$$\boxed{I_{in} = 0.02 \text{ mA}} \text{ ANS}$$



Op-Amp Subtractor

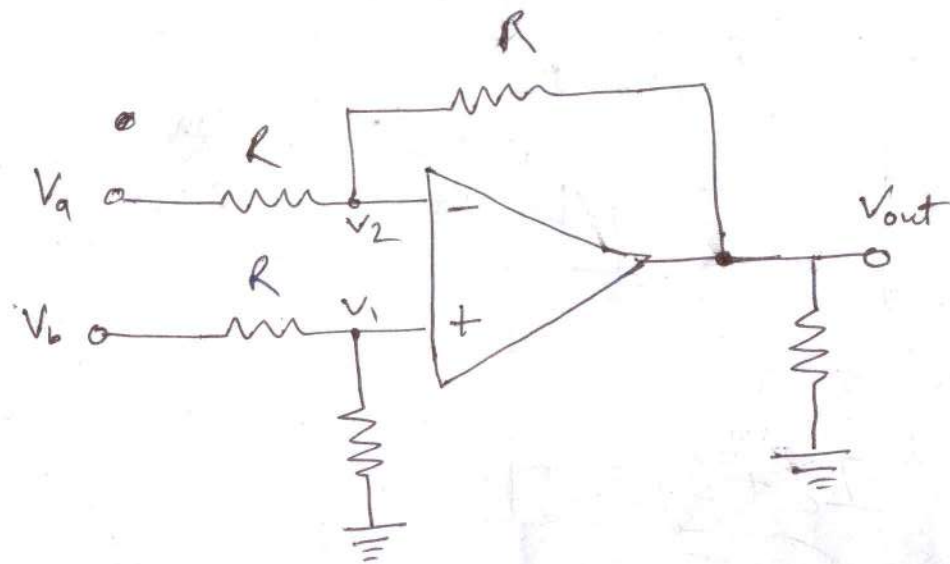

$$\text{or } V_{out} = -\frac{R}{R} (V_a - V_b)$$

$$\boxed{V_{out} = V_a - V_b}$$

Adder or Summing Amp.

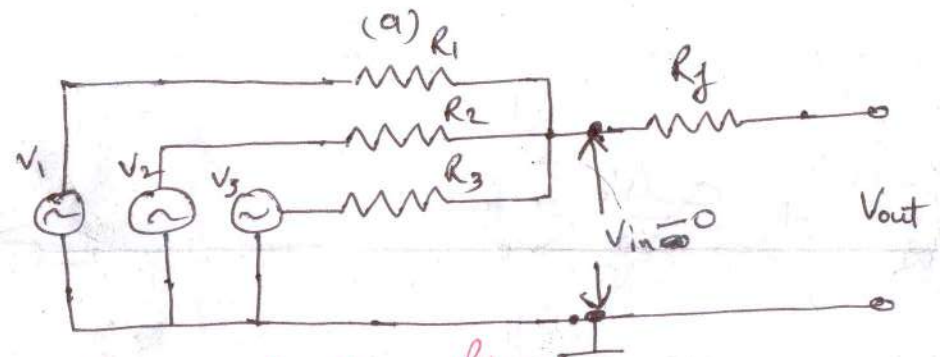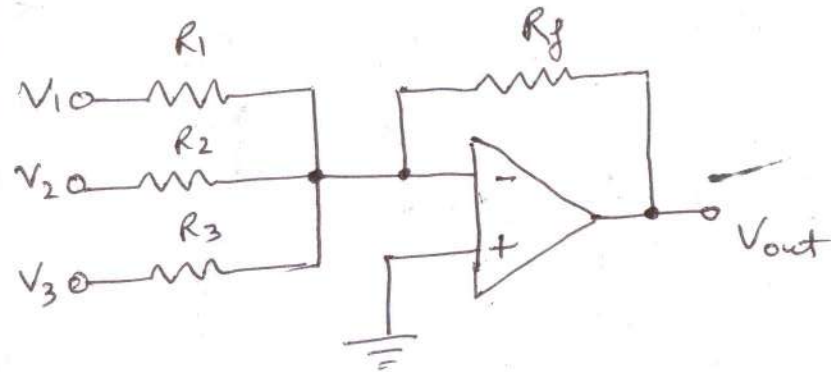


$$V_i = -A_f V_o = \frac{R_f}{R} V_o$$

$$V_{out} = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

$$\text{if } R_1 = R_2 = R_3 = R_f$$

$$\text{then } V_{out} = -(V_1 + V_2 + V_3)$$

Integrator

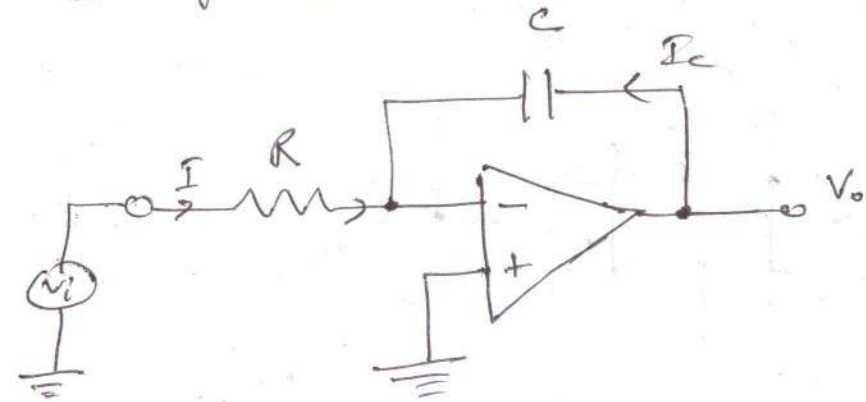

$$I + I_c = 0$$

$$\frac{V_i - 0}{R} + C \frac{dV_o}{dt} = 0$$


$$\frac{V_i}{R} + C \frac{dV_o}{dt} = 0$$

$$C \frac{dV_o}{dt} = -\frac{V_i}{R}$$

$$\frac{dV_o}{dt} = -\frac{V_i}{RC}$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

Differentiator

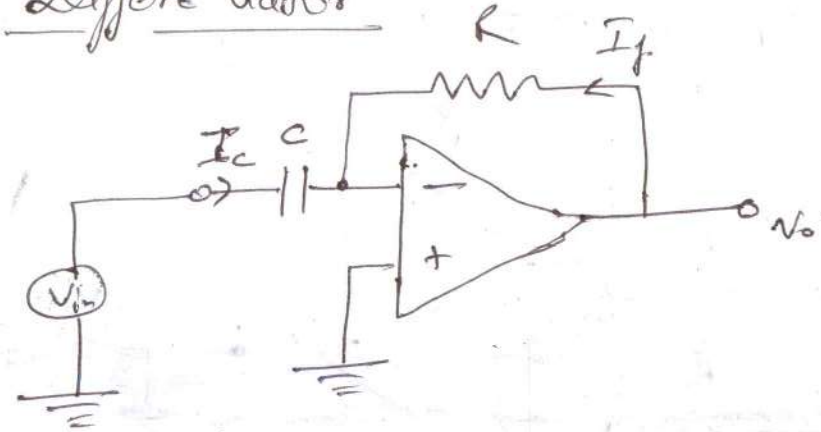

$$I_c + I_f = 0$$

$$C \frac{dV_i}{dt} + \frac{V_o}{R_f} = 0$$

$$\frac{V_o}{R_f} = -C \frac{dV_i}{dt}$$

$$V_o = -R_f C \frac{dV_i}{dt}$$

Comparator:

- A comparator compares a voltage signal applied to one input of the op-amp with a known voltage, called reference voltage applied at the other input.
- In its simplest form, the comparator consists of an op-amp ~~operated~~ operated in open loop.
- In this configuration op-amp produces one of the two saturation voltages, namely, positive or negative at the output of op-amp.

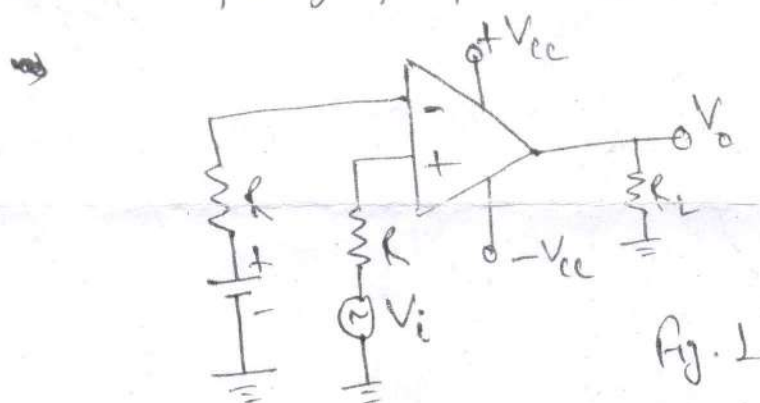


Fig. 1


- Fig 1 shows an op-amp configured for use as a non-inverting comparator.
- A fixed reference voltage V_{ref} is applied to (-) input and a time varying signal V_i is applied to (+) input.
- When the non-inverting input V_i is less than the reference voltage V_{ref} , the output voltage V_o is at $-V_{sat} \approx -V_{EE}$.

②

→ When V_i greater than V_{ref} , the output voltage V_o is at $+V_{sat} \approx +V_{cc}$

→ Thus the output V_o changes from one saturation level to another depending on the voltage difference between V_i and V_{ref}

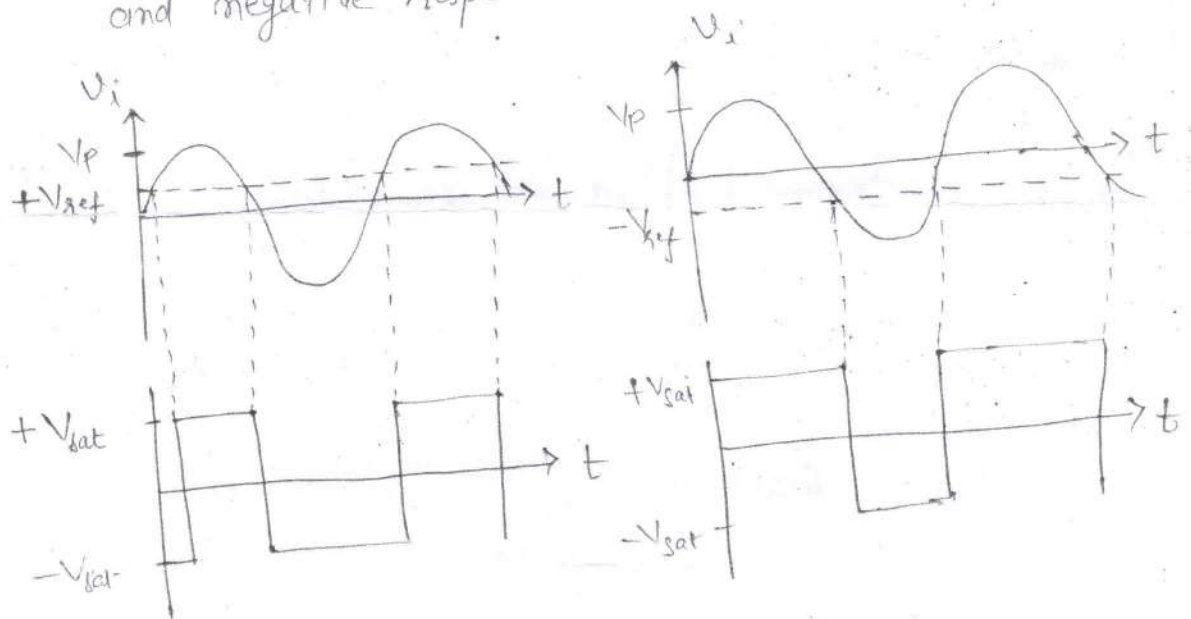→ Fig 2 (a) and (b) show the input and output waveform of the comparator when V_{ref} is positive and negative respectively.




Exp Design an adder circuit using an op-amp to get o/p expression as ①

$$V_o = -(V_1 + 10V_2 + 100V_3) \quad \text{--- ①}$$

where V_1, V_2 and V_3 are the i/p

Given that $R_f = 100\text{ k}\Omega$.

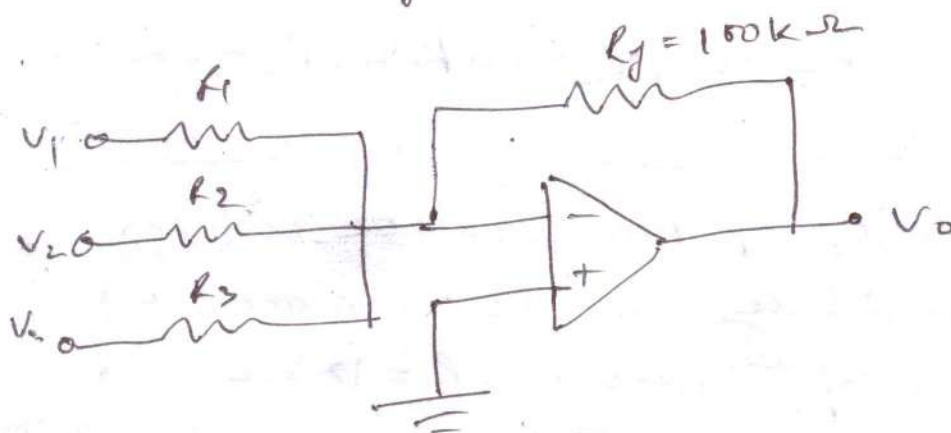

$$V_o = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right] \quad \text{--- ②}$$

Comparing the above expression.

(i) $\frac{R_f}{R_1} = 1$, (ii) $\frac{R_f}{R_2} = 10$

(iii) $\frac{R_f}{R_3} = 100$

(i) $R_f = R_1 = 100 \text{ k}\Omega$

(ii) $\frac{R_f}{R_2} = 10 \Rightarrow R_2 = \frac{R_f}{10} = \frac{100}{10} = 10 \text{ k}\Omega$

(iii) $\frac{R_f}{R_3} = 100 \Rightarrow R_3 = \frac{R_f}{100} = \frac{100}{100} = 1 \text{ k}\Omega$

$R_1 = 100 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega, R_3 = 1 \text{ k}\Omega$

Ex An opamp has feedback resistor $R_f = 12 \text{ k}\Omega$ and the resistance on the input sides are $R_1 = 12 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_3 = 3 \text{ k}\Omega$. The corresponding i/p are $V_1 = +9 \text{ V}$, $V_2 = -3 \text{ V}$, $V_3 = -1 \text{ V}$. Non-inverting terminal is grounded. Calculate the o/p voltage.

Sol

$$V_o = -R_f \left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

$$= -12 \left[\frac{9}{12} - \frac{3}{2} - \frac{1}{3} \right]$$

$$= -[9 - 18 - 4]$$

$$= 18 + 4 - 9 = 13 \text{ V.}$$

Ex Sketch the circuit of summer using op-amp to get

$V_o = -V_1 + 2V_2 - 3V_3$

Sol

$$V_o = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

~~Comparing (1) and (2)~~

$V_o = -(V_1 - 2V_2 + 3V_3)$ — (1)

By comparing.


$\frac{R_f}{R_1} = 1, \frac{R_f}{R_2} = 2, \frac{R_f}{R_3} = 3$

Taking $R_f = 6 \text{ k}\Omega$.

$R_1 = R_f = 6 \text{ k}\Omega$

$R_2 = \frac{R_f}{2} = 3 \text{ k}\Omega$

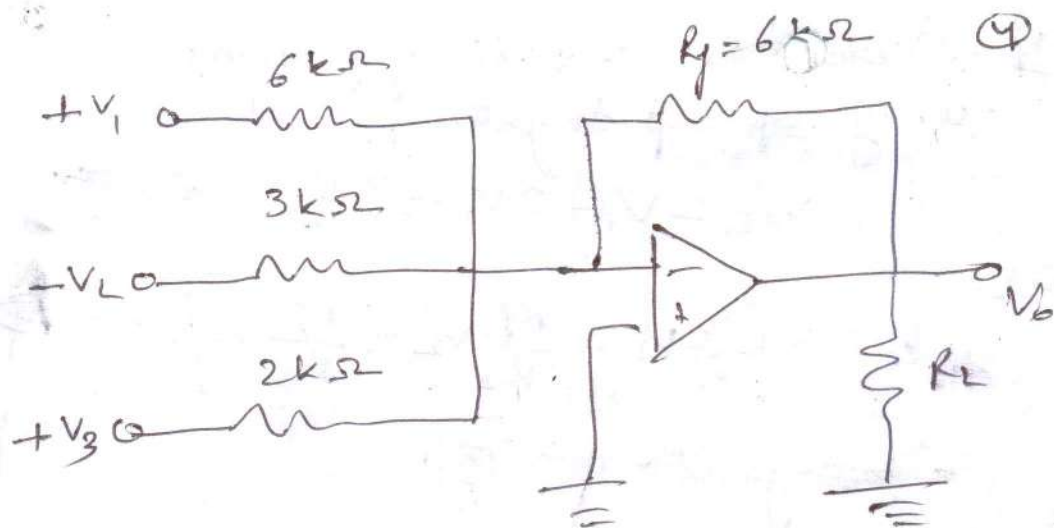$R_3 = \frac{R_f}{3} = 2 \text{ k}\Omega$



~~Find~~ Relative ckt to

Exp Realize a ckt to obtain

①

$$V_o = -2V_1 + 3V_2 + 4V_3$$

Use minimum value of resistance as
10 k Ω .

sol

$$V_o = -\left[\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right] \quad \text{--- (1)}$$

Given

$$V_o = -[2V_1 + 3V_2 + 4V_3] \quad \text{--- (2)}$$

By Comparing.

$$\frac{R_f}{R_1} = 2, \quad \frac{R_f}{R_2} = 3, \quad \frac{R_f}{R_3} = 4$$

$$\cancel{R_3} = \frac{R_f}{4} =$$

$$R_f = 4R_3 = 4 \times 10 = 40 \text{ k}\Omega$$

$$R_1 = \frac{40}{2} = 20 \text{ k}\Omega$$

$$R_2 = \frac{40}{3} = 13.33 \text{ k}\Omega$$

$$R_3 = \frac{40}{4} = 10 \text{ k}\Omega.$$

